



OSNOVE DIGITALNE ELEKTRONIKE

Bistabili

Zdravko Kunić
zdravko.kunic@algebra.hr



Bistabili

Ishod učenja 7 - Uvod u sekvencijske sklopove

Sadržaj predavanja


- Sekvencijski sklopovi
- Asinkroni i sinkroni bistabili
- Tipovi bistabila (RS, JK, T, D)
- Upravljanje bistabilima (CP)
- Upravljanje sekvencijskim sklopovima razinom i bridom

Uvod

- Kombinaijski sklopovi nemaju svojstvo pamćenja
- Izlaz postoji samo kad postoji i ulaz
- Da bi logički sklop mogao pamtitu ulaznu vrijednost varijable mora imati **logičku povratnu vezu**



Struktura sekvencijskog sklopa

 - Kombinaijski dio (KS)
- Memorija (M)
 - dva stabilna stanja omogućuju pamćenje binarne vrijednosti



Bistabil


 
 
- Sklop s dva stabilna stanja
- Stanje se može promijeniti samo pomoću vanjskog impulsa
- Može pohraniti (zapamtiti) jedan bit informacije
- U širokoj je upotrebi u digitalnoj logici i računalnoj memoriji




Osnovni spoj bistabila

Bistabil ostvaren logičkim sklopovima:

   - električka i "logička" povratna veza
- Logička struktura za pohranu informacija







Invertor s NI i NILI funkcijama

 


- Univerzalne funkcije omogućuju upravljanje bistabilom

    Bistabil ostvaren NLI logičkim sklopovima



 Bistabil ostvaren NLI logičkim sklopovima




(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

 (b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved

Bistabil ostvaren NLI logičkim sklopovima




(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

 (b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved

Bistabil ostvaren NLI logičkim sklopovima



(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved


Simbol bistabila

Izlazi:

- Q izlaz
- \bar{Q} komplementarni izlaz



Ulazi:

 - **S** [set] postavljanje $Q = 1$
- **R** [reset] "brisanje"! $Q = 0$







Ponašanje bistabila

  
- Djelovanje impulsa na jednostavni SR bistabil



Bistabil ostvaren NI logičkim sklopovima

    

 $\bar{S}\bar{R}$ bistabil ostvaren NI logičkim sklopovima




(a) Logic diagram

\bar{S}	\bar{R}	Q	\bar{Q}	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined

 (b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved

$\bar{S}\bar{R}$ bistabil ostvaren NI logičkim sklopovima




(a) Logic diagram

\bar{S}	\bar{R}	Q	\bar{Q}	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined

 (b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved

$\bar{S}\bar{R}$ bistabil ostvaren NI logičkim sklopovima




(a) Logic diagram

\bar{S}	\bar{R}	Q	\bar{Q}	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined

(b) Function table


Copyright ©2016 Pearson Education, All Rights Reserved

Vremenski odziv NI sklopa

 


U_u = ulazni napon
 U_{izl} = izlazni napon
 t_d = vrijeme kašnjenja (time of delay)


a) Linearna promjena

 

b) Idealizirana promjena

 


Vremenski odziv bistabila

 

Sklop je osjetljiv na trajanje pobude (okidnog impulsa):
 $t > 2t_D$

Moguć HAZARD!

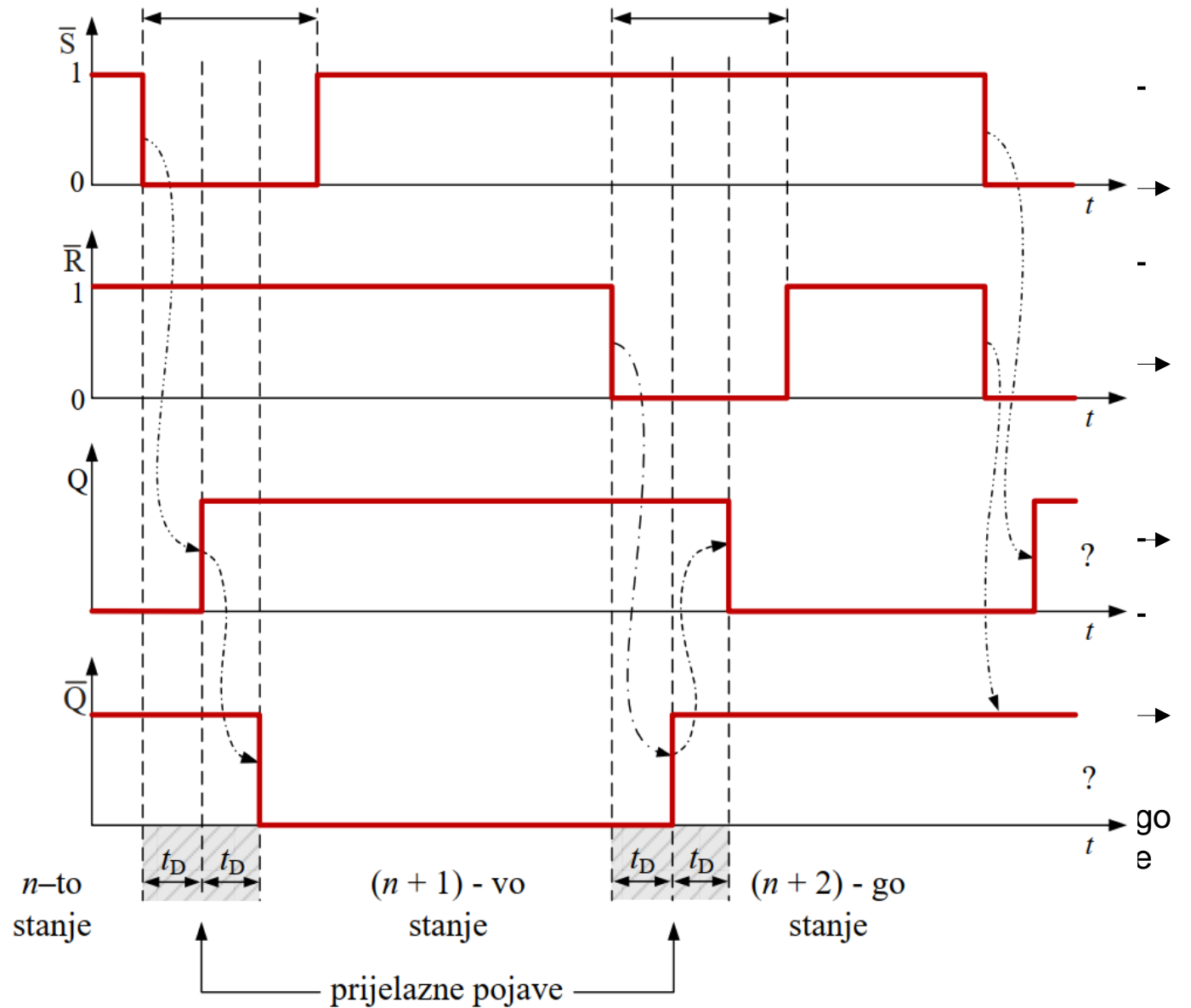


Sekvencijski sklopovi


- Mijenjaju stanje pod utjecajem impulsa takta
- Stanje sklopa se može promijeniti samo u određenim trenucima, čime se izbjegavaju negativni učinci prijelaznih pojava
- Pohranjena binarna informacija definira stanje sekvencijskog sklopa u promatranom trenutku.
- Sekvencijski sklop prima binarne informacije iz svog okruženja putem ulaza
 - Binarna vrijednost izlaza određena je stanjem ulaznih varijabli i pohranjenim stanjem

Sinkroni bistabil

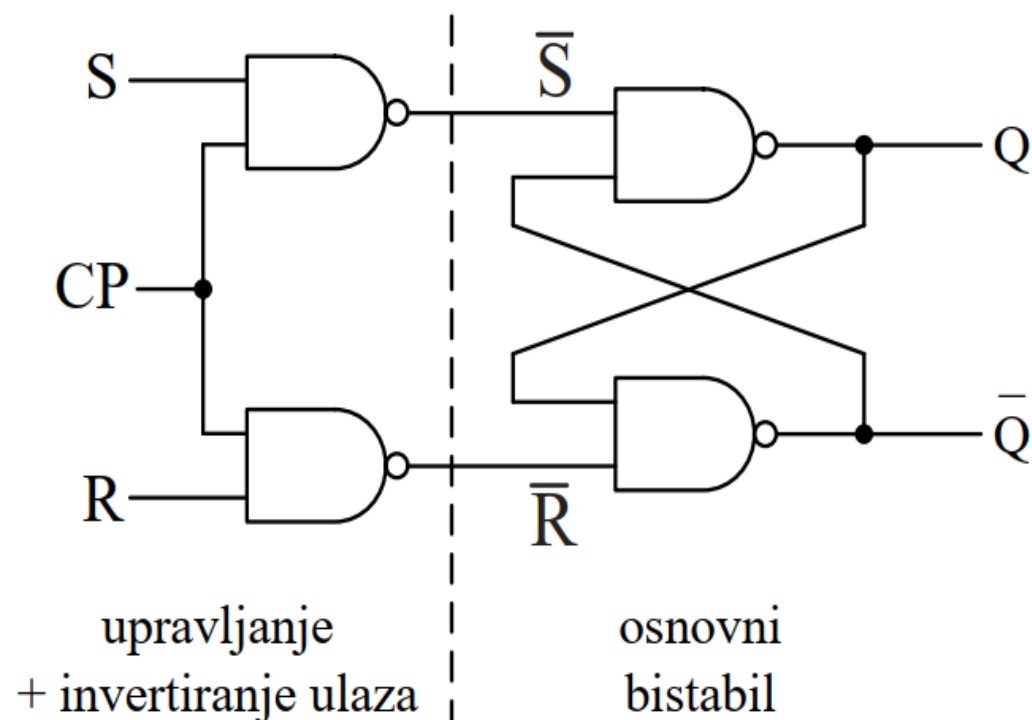- Na poseban ulaz sinkronog bistabila se dovode sinkronizacijski impulsi **CP** (engl. Clock Pulses)
- Promjena stanja bistabila je moguća samo kad je $CP=1$
- Ulazi su invertirani, odnosno $\bar{S} \bar{R} \rightarrow S R$



Sinkroni bistabil

 


(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

(b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved

Sinkroni bistabil

 

(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

(b) Function table

Copyright ©2016 Pearson Education, All Rights Reserved

Sinkronizacija okidanja bistabila

Asinkroni bistabil



- reagira na promjenu impulsa čim se impuls pojavi na ulazu u sklop, što daje pogrešan rezultat ako se ulazni impulsi ne dovode istovremeno na ulaz

Sinkroni bistabil

- verzija asinkronog bistabila s dodatnim ulazom CP
- Na ulaz CP (eng. *Clock Pulse*) se dovode sinkronizacijski impulsi konstantne frekvencije
- CP sinkronizira promjene stanja na ulazima bistabila


Sinkronizacija okidanja bistabila

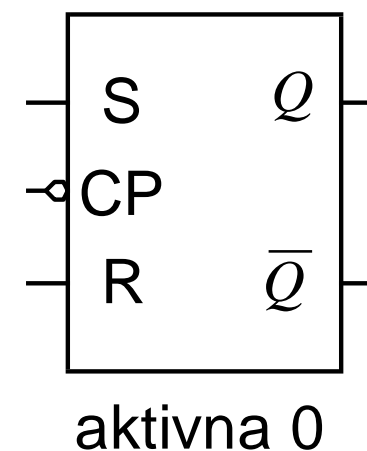 - konceptualno: *diskretizacija* vremena
- značajno olakšava razmatranje sekvencijskih sklopova
 - sekvencijski se problem svodi na kombinacijski
- obično se razmatra prijelaz iz stanja (n) u stanje (n+1)
 - prije (n), odnosno poslije nailaska CP impulsa (n+1)
- aktivna razina okidanja bistabila može biti 0 ili 1
 - aktivna razina 0 se označava kružićem na CP ulazu





Dodatni asinkroni ulazi

 - Omogućuju zaobilaznje sinkronizacijskih impulsa
 - direktni ulazi (\overline{S}_d , \overline{C}_d)
 - Aktivna razina je 0
 - dominiraju nad sinkronim ulazima S i R
- Potencijalni problem:
 - za vrijeme CP aktivna pobuda putem sinkronih i asinkronih ulaza može izazvati hazard





Djelovanje impulsa na SR bistabil

Jednostavni
SR bistabil

  

Upravljeni
SR bistabil

  

Tipovi bistabila

- **SR** bistabil [set] [reset]
 - osnovna funkcionalnost
- **JK** bistabil*
 - proširena funkcionalnost: "univerzalni" bistabil
- **T** bistabil [toggle]
 - (samo) promjena stanja
- **D** bistabil [delay]
 - (samo) pamćenje 1 bita informacije

* JK bistabil je dobio ime po Texas Instrumentsovom inženjeru Jacku Kilbyju koji ga je osmislio 1958. godine

SR bistabil


Tablica stanja

Q_n	S	R	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?, X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?, X

Sažeta tablica stanja

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	X

Dijagram stanja

 


SR bistabil

Q_n	S	R	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?, X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?, X

Tablica uzbude predstavlja kombinaciju koja je potrebna da sklop prijeđe iz stanja Q_n u stanje Q_{n+1}

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

 


Uvjet $S \cdot R = 0$ omogućuje korištenje X u K-tablici

$$\text{Jednadžba stanja: } Q_{n+1} = S + \bar{R} \cdot Q_n$$

JK Bistabil („univerzalni” bistabil)

Rješava problem zabranjenih kombinacija na R i S ulazima

 - za JK = 11 bistabil mijenja stanje (engl. *toggle*)
- Izlazi se koriste za upravljanje vlastitim ulazima





Sažeta tablica:

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

JK bistabil

Primjer vremenskog dijagrama

  

T = toggle


JK bistabil

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Tablica uzbude

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Dijagram stanja

 


JK bistabil

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Tablica uzbude


Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

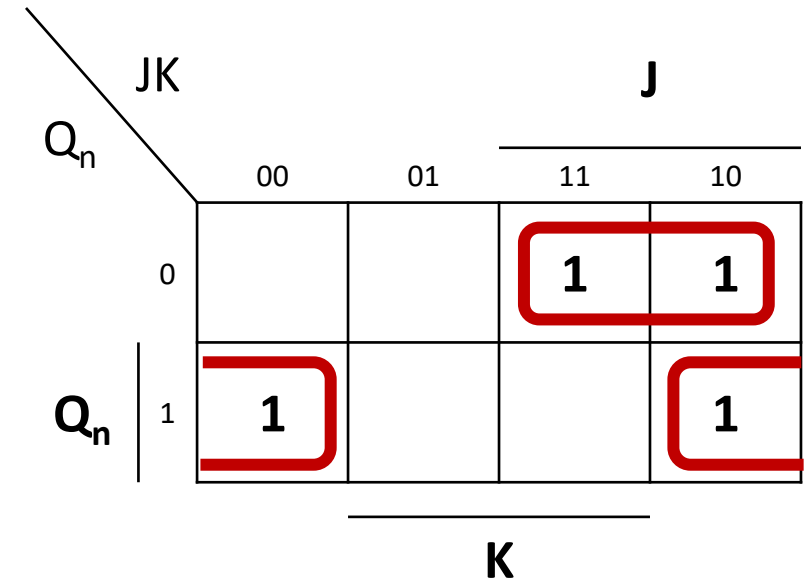

Jednadžba stanja:

$$Q_{n+1} = J \cdot \bar{Q}_n + \bar{K} \cdot Q_n$$


JK bistabil izveden pomoću NI sklopova

 

CP = 1 ne smije trajati predugo radi opasnosti od osciliranja (neprekidne promjene stanja)

Suprotstavljeni zahtjevi za trajanje CP

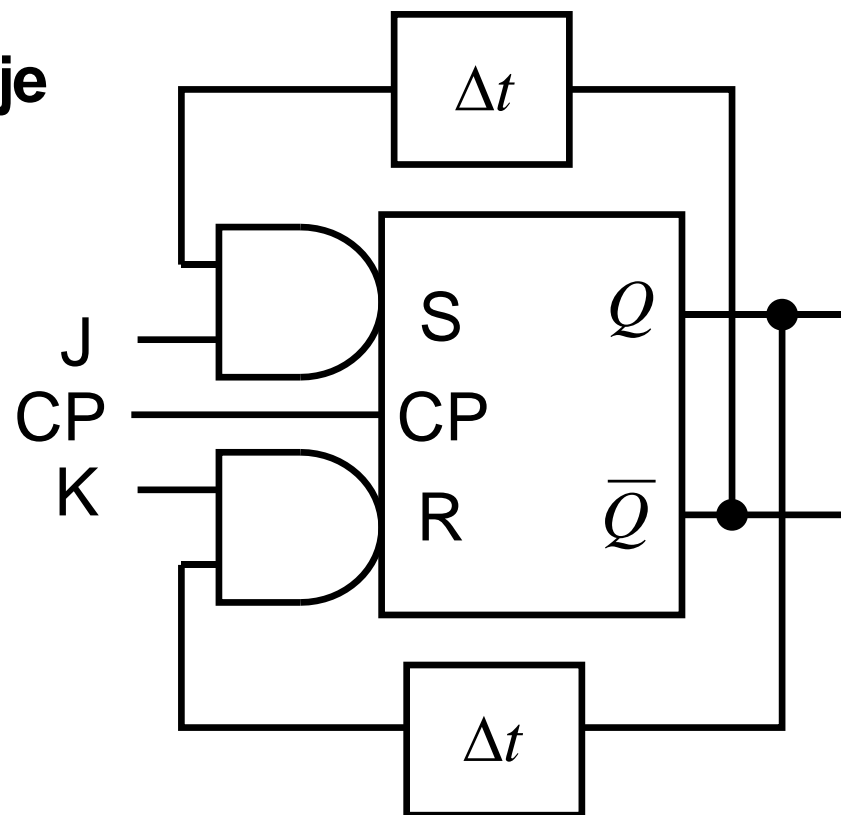
- Dužina CP impulsa mora biti:
 - dovoljno **duga** da bistabil **promijeni stanje**
 - dovoljno **kratka** da bistabil **ne zaoscilira**
- Moguća rješenja:
 - odgovarajuća kašnjenja u petlji povratne veze
 - poboljšano upravljanje djelovanjem na CP



T bistabil (od engl. *Toggle*)

Međusobnim spajanjem J i K ulaza dobivamo **T bistabil**

 - Uz $T = 0$, bistabil mijenja stanje sa svakim CP impulsom
- Tipično se primjenjuje za brojanje impulsa (u sklopovima brojila)



Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

T bistabil

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

T	Q_{n+1}
0	Q_n
1	$\overline{Q_n}$

T bistabil

Tablica stanja

Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0



Tablica uzbude

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Sažeta tablica stanja

T	Q_{n+1}
0	Q_n
1	$\overline{Q_n}$


Q_n	T
Q_n	1
$\overline{Q_n}$	1

  

$$Q_{n+1} = T \cdot \overline{Q_n} + \overline{T} \cdot Q_n$$

D bistabil (od engl. *Delay*)

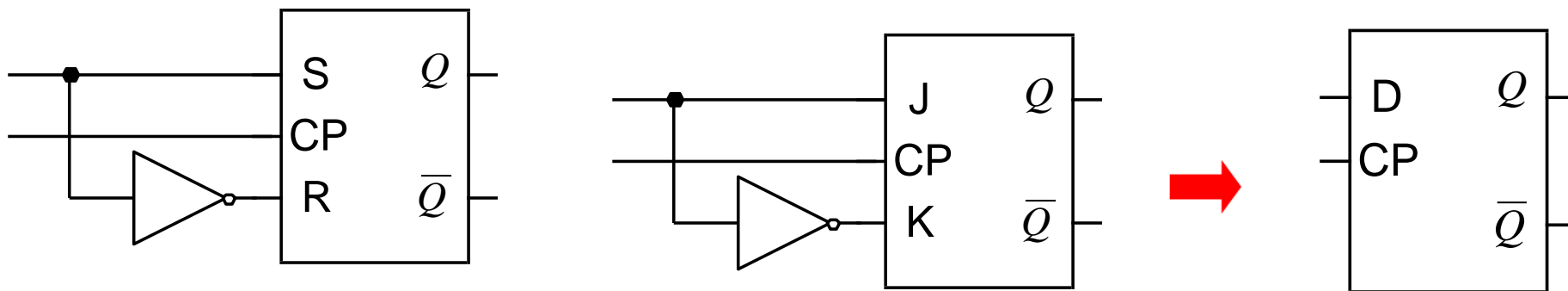
- Međusobnim spajanjem ulaza i invertiranog ulaza na RS ili JK bistabil dobivamo **D bistabil**
- D bistabil pamti (memorira) podatak (jedan ulazni bit)
- Primjenjuje se za:
 - pohranu podataka (registar)
 - kašnjenje (engl. *delay*) za 1 x CP



D bistabil

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

D	Q^{n+1}
0	0
1	1

 

D bistabil

Tablica stanja

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1



Tablica uzbude

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Sažeta tablica stanja

D	Q^{n+1}
0	0
1	1

		D	
		0	1
Q_n	0		1
	1		1

 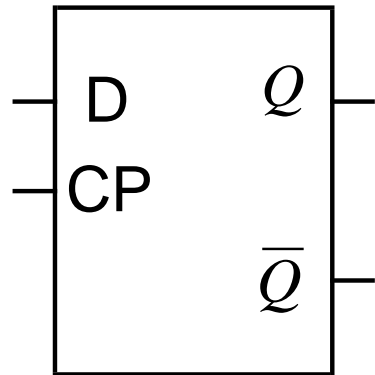

$$Q_{n+1} = D_n$$

Prevencija osciliranja JK bistabila

Moguća rješenja za poboljšanje upravljanja putem CP:

- **Razinom okidani bistabil** (engl. *latch*) - daje odziv na svojim izlazima kod **promjene ulazne razine**
- **Bridom okidani bistabil** (engl. *flip-flop*) daje odziv na ulazne promjene samo u vremenskim trenucima **promjene signala takta**
 - Uzima uzorke signala s ulaza samo na bridovima signala takta
 - Stanja izlaza se mijenjaju isključivo kao rezultat pojave brida signala takta

Dvostruki bistabil (*master-slave flip-flop*)

Upravljanje razinom CP:

1. $CP = 0$


- glavni (G) i pomoćni (P) bistabil su povezani ($CP=1$)

2. $CP = 1$

- u glavni bistabil se upisuje novi sadržaj

 3. $CP = 0$

- sadržaj glavnog bistabila se prenosi u pomoćni bistabil





Razinom okidani bistabil

Princip rada:

- t_1 : CP izlazi iz područja **0**:
prekid veze G i P
- t_2 : CP ulazi u područje **1**:
uspostavljanje veze ulaza i G,
upis podataka u G
- t_3 : CP izlazi iz područja **1**:
prekid veze ulaza i G
- t_4 : CP ulazi u područje **0**:
uspostavljanje veze G i P,
upis podataka iz G u P

Osciliranje je onemogućeno

  

Bridom okidani bistabil *(edge-triggered flip-flop)*

Upravljanje **bridom** CP:

- Bistabil ignorira postojano stanje CP-a - okida samo tijekom tranzicije stanja $1 \rightarrow 0$ ili $0 \rightarrow 1$, ovisno o izvedbi


Osnovna ideja:

- na jedan od bridova impulsa CP generirati **kratki impuls** koji će propustiti ulaze
- više mogućih izvedbi
 - korištenje **CR mreže**
 - korištenje **kašnjenja u logičkim sklopovima**
 - kombiniranje **većeg broja osnovnih bistabila**

Kreiranje impulsa CR mrežom


Mreža CR - deriviranje impulsa CP

- nije prikladno za integriranu izvedbu

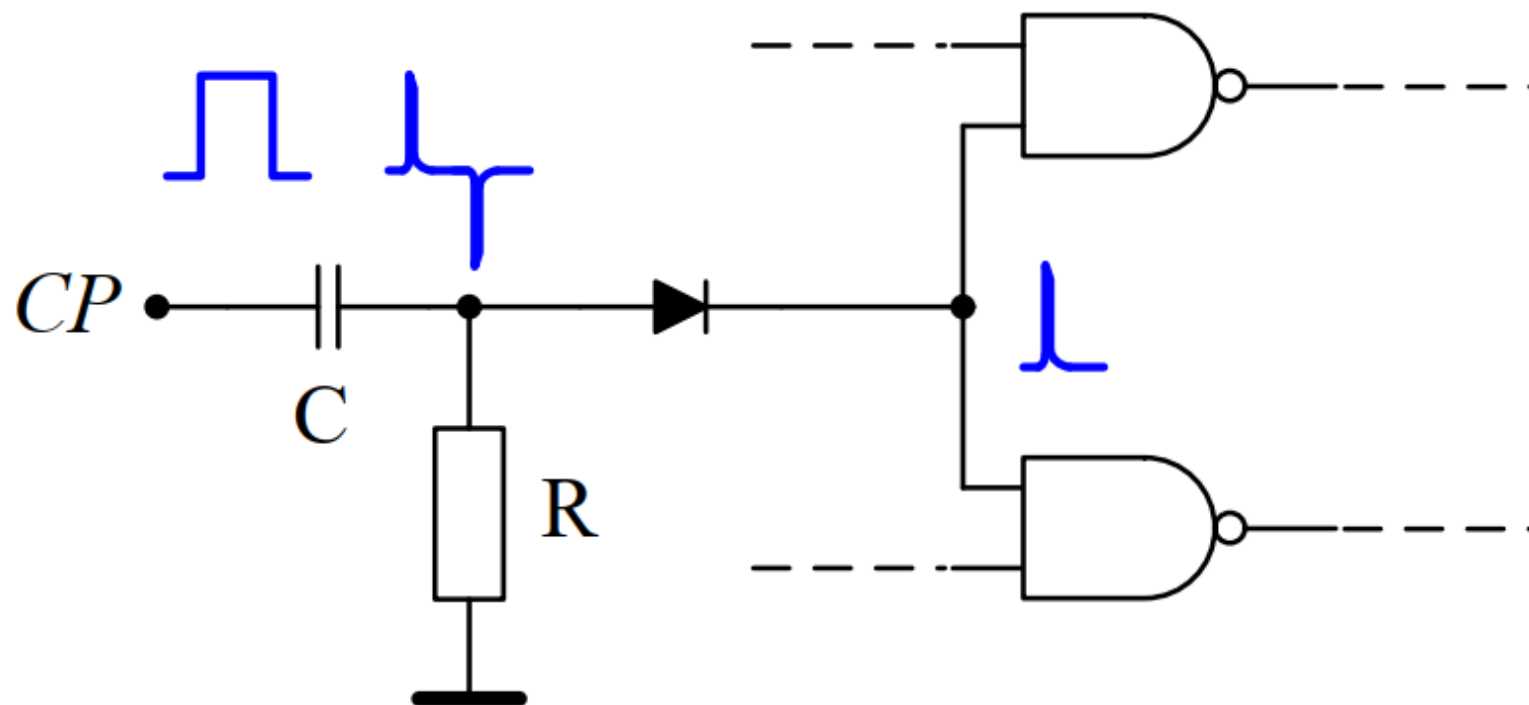


Kreiranje impulsa kašnjenjem

 Korištenje kašnjenja u logičkim sklopovima





 Na rastući brid impulsa CP generira se impuls trajanja t_d





Sklopovi za detekciju brida


- Sklop za detekciju padajućeg brida

  


- Sklop za detekciju rastućeg brida

  






Bridom okidani JK bistabil

 

 
Simbolički prikaz okidanja negativnim bridom:




Usporedba upravljanja razinom i bridom

     

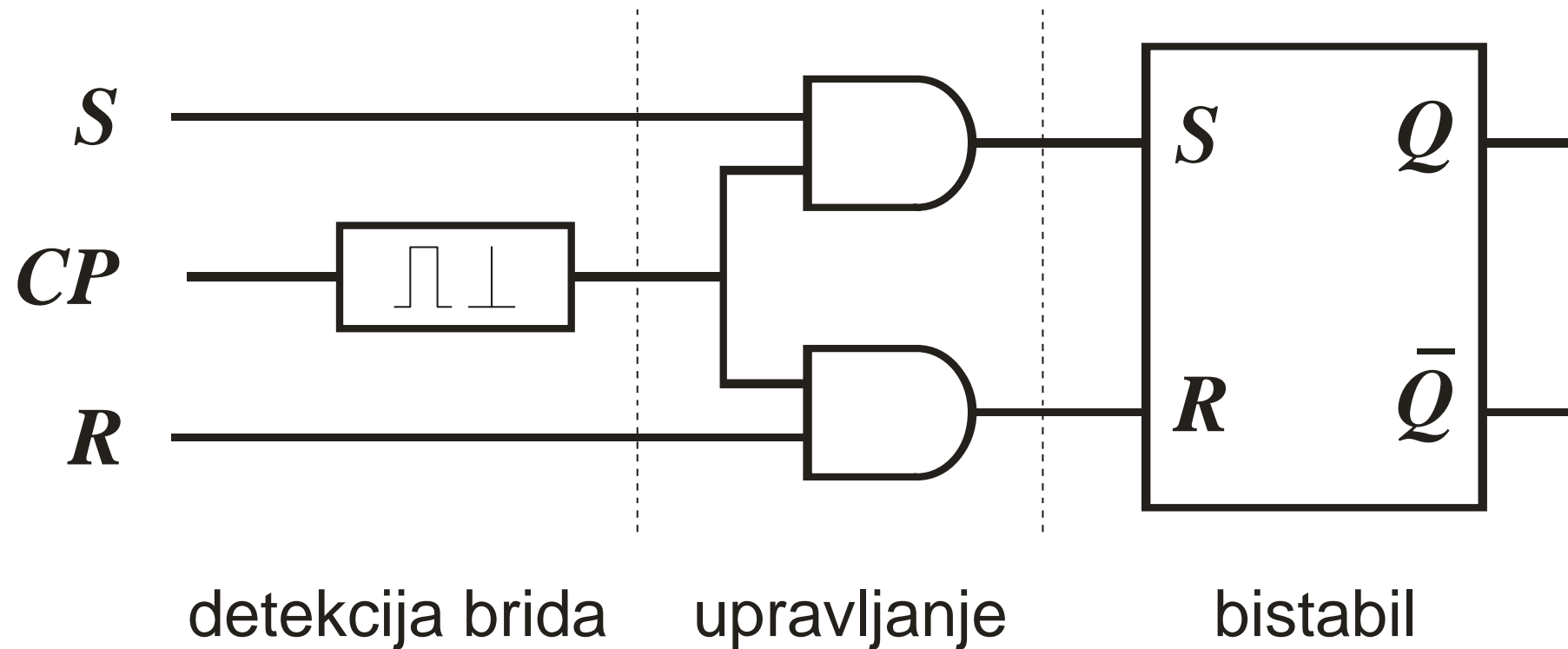Logička shema bridom upravljano SR-bistabila



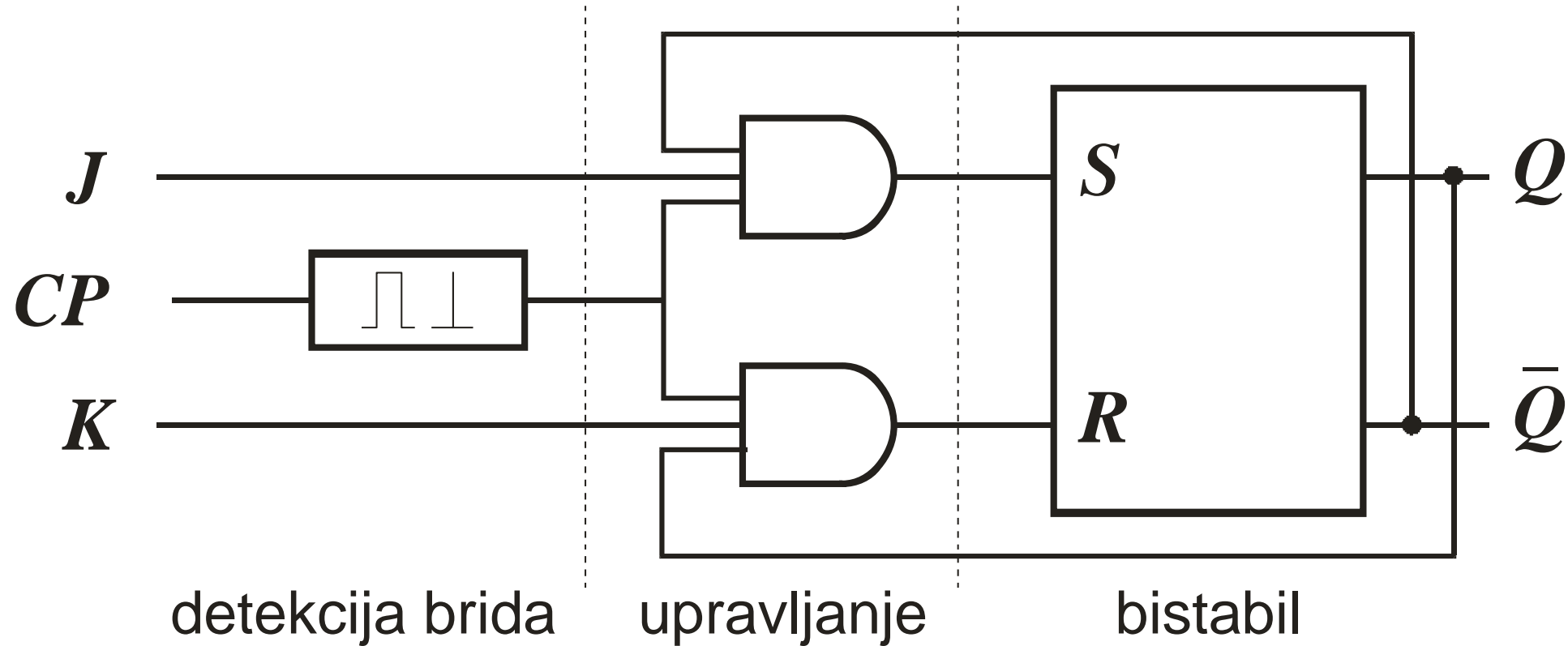Logička shema bridom upravljano JK-bistabila






Bistabili




LITERATURA:

- Uroš Peruško: Digitalni sustavi
 - Str. 165 - 198


SR

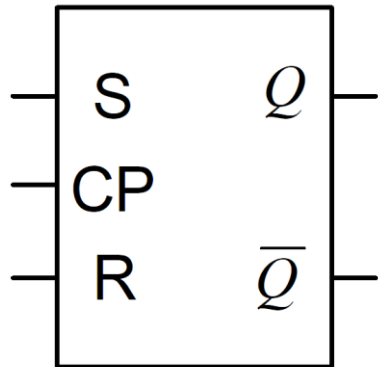


JK

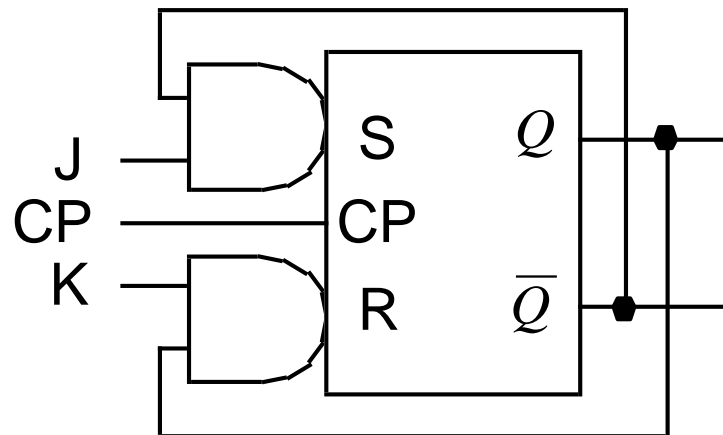


T

 


D

 


D

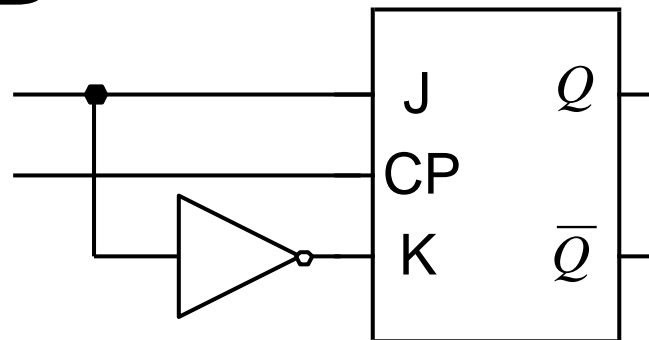


SR

 


T




 


JK

 

D

 

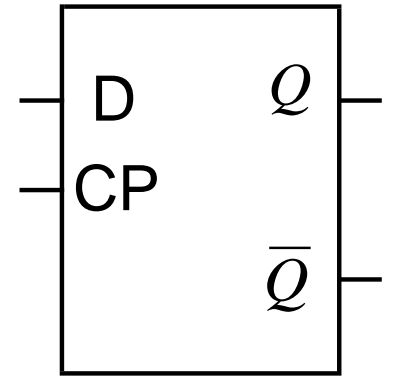  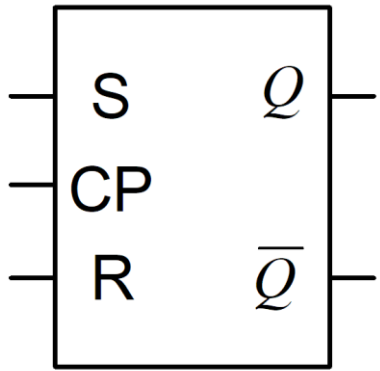

Q_n	S	R	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

T	Q_{n+1}
0	Q_n
1	$\overline{Q_n}$

D	Q^{n+1}
0	0
1	1